
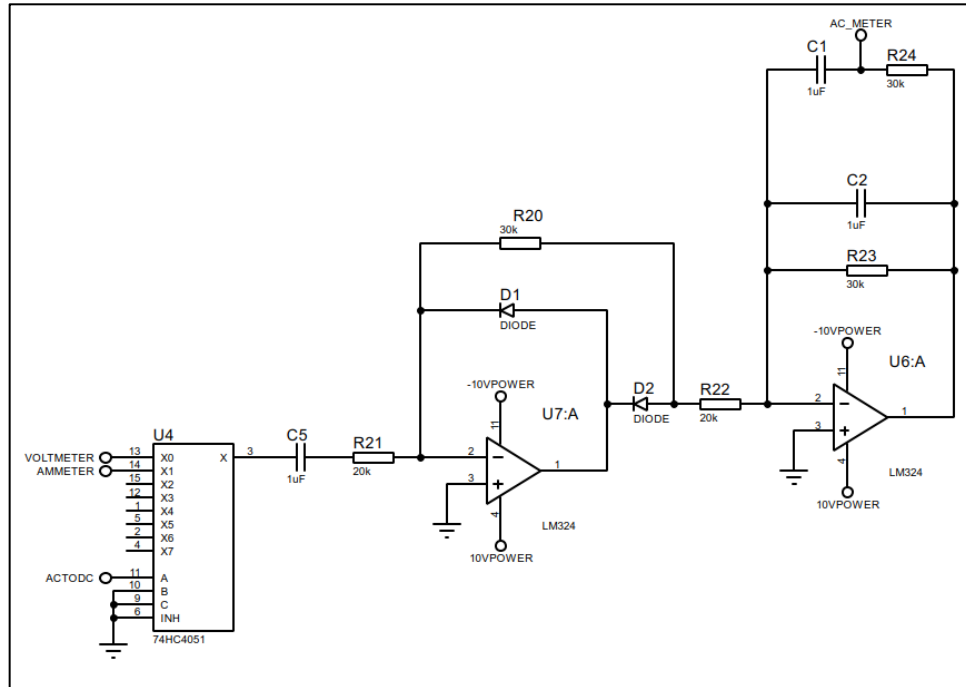




AVR Circuit

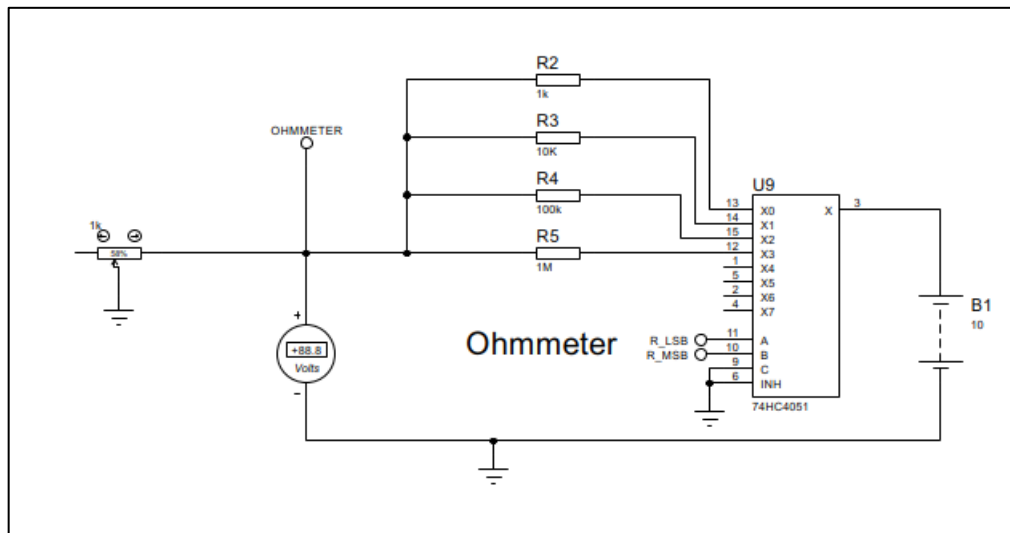


AC to DC Circuit




Ohmmeter Circuit

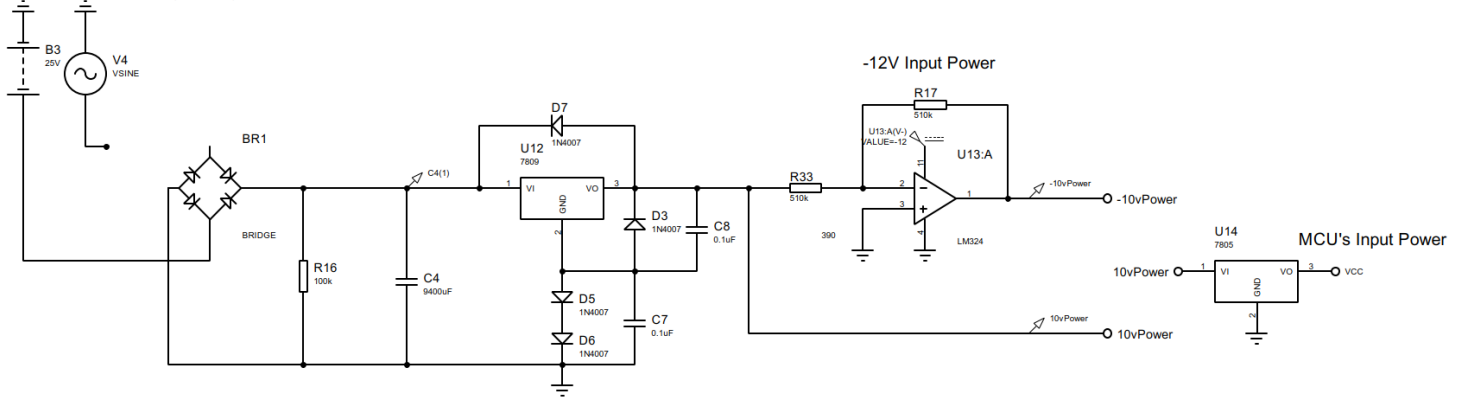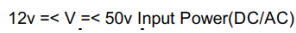

Power Circuit

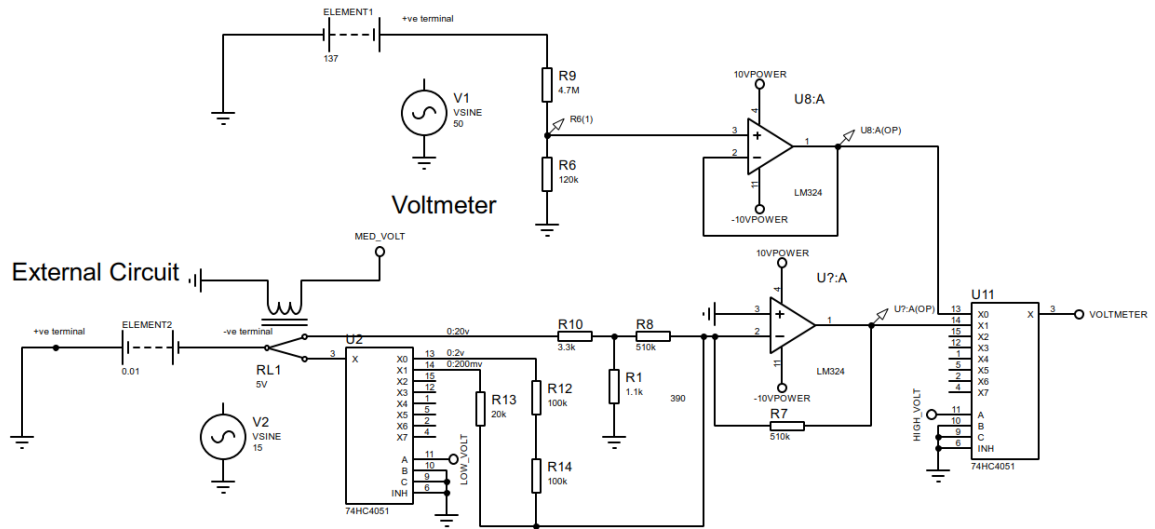

Voltmeter Circuit

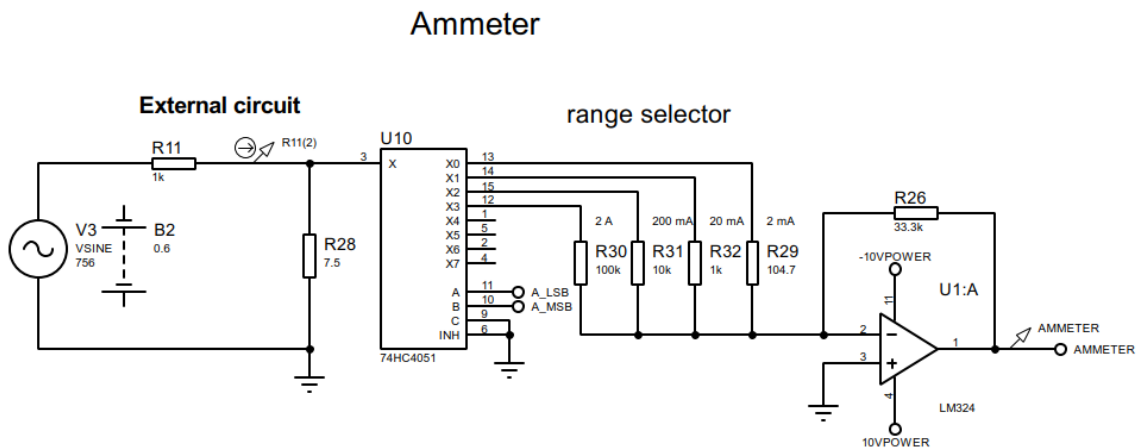

Ammeter Circuit